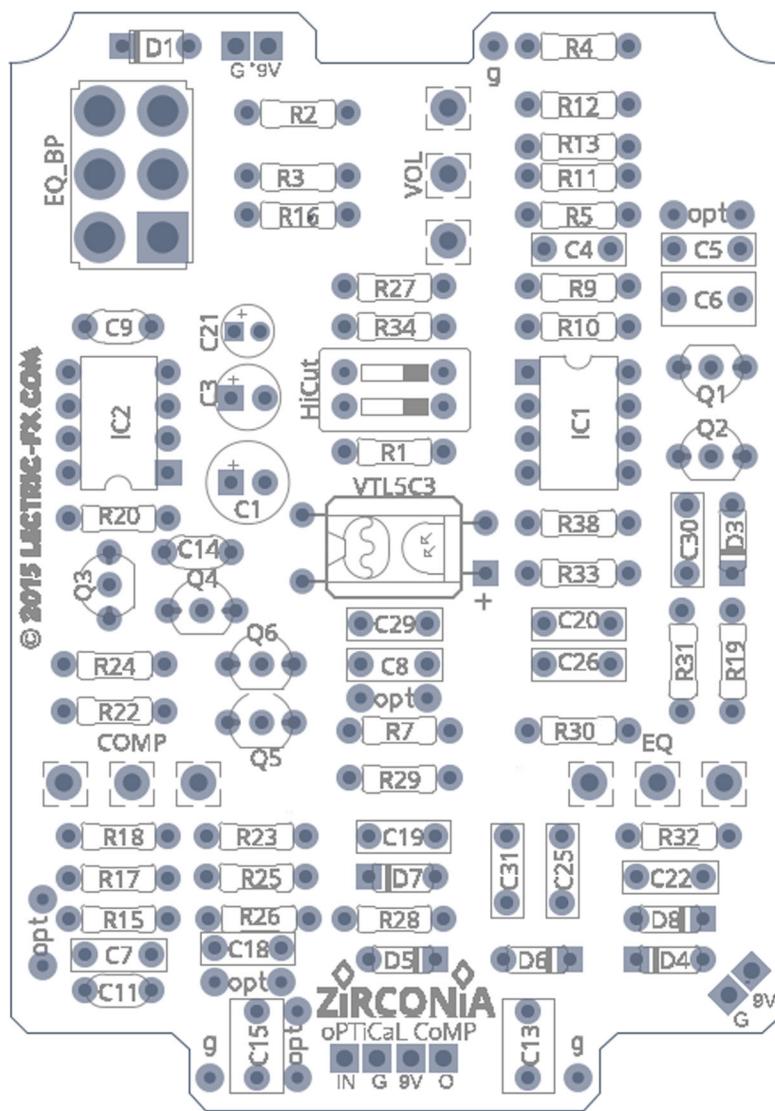




© LECTRIC-FX.COM

oPTiCaL CoMP



Changes for V1.1: Pots and switch have been moved.

The ZiRCOniA is an optical compressor using a VTL5C3 vactrol (or similar) that includes a tilt style EQ, external EQ-bypass toggle, and internal Hi Cut switch.

The controls are:

Volume- Sets the output level.

EQ- This is a "tilt" style EQ that cuts bass as the treble is increased (CW) and conversely cuts treble as bass is increased (CCW).

COMP- Increases the amount of compression and sustain.

The Hi Cut dipswitch uses the bottom dip only. The top switch is floating. Also, please note the "+" symbol near the vactrol's silkscreen, which indicates the position of the positive leg.

# ZiRCONiA Bill of Materials

Part #'s/Values

R1	100R	C1	100u	Q1	2N3904
R2	10k	C3	47u	Q2	2N3904
R3	10k	C4	5n6	Q3	2N3904
R4	100R	C5	5n6	Q4	2N3904
R5	15k	C6	330n	Q5	2N3904
R7	22k	C7	100n	D1	1N4001
R9	15k	C8	100n	D3	1N4148
R10	47k5	C9	100p	D4	1N4148
R11	47k5	C11	100p	D5	1N4148
R12	47k5	C13	1u	D6	1N4148
R13	47k5	C14	100p	D7	1N4148
R15	1M	C15	330n	D8	1N4148
R16	475R	C18	100n	IC1	LM358
R17	475k	C19	10n	IC2	OP275
R18	475k	C20	10n	VACTROL	VTL5C3
R19	3k3	C21	2u2	HiCut	DIP2
R20	6k4	C22	100n	SW2	DPDT
R22	100R	C25	3n3	VOL	100KA
R23	475k	C26	15n	COMP	100KB
R24	22k	C29	3n3	EQ	50KB
R25	100k	C30	100n		
R26	1k	C31	100n		
R27	3k3				
R28	475r				
R29	220k				
R30	475k				
R31	100k				
R32	220k				
R33	100k				
R34	475k				
R38	10k				

Cap/Resistor Totals

3	100R	3	100p
2	475R	4	820p *
1	1k	2	3n3
2	3k3	2	5n6
1	6k4	2	10n
4	10k	1	15n
3	15k	6	100n
2	22k	2	330n
5	47k5	1	1u
2	100k	1	2u2
3	220k	1	47u
4	475k	1	100u
1	1M		

\* Optional parallel caps for C6, C7, C8, C15, and C18. See explanation below.

There are 4 spaces on the pcb labeled "opt". These are where you would install the 4x 820p caps if you so wish. They aren't crucial to the sound, so we omitted them from the schematic.

Some of the resistor values are a bit odd. feel free to sub the closest value without fear.  
Example- a 470R can be used in place of 475R.


The VTL5C3 is the recommended vactrol, but I used the MI1210CLF-R (smallbear item SKU: 2510M) with great results. It is possible an NSL-32, or even a home rolled vactrol could work, but I have not tested this.

## Bill of Materials (BASS version)

R1	100R	C1	100u	Q1	MPSA18
R2	10k5	C3	47u	Q2	2N5088
R3	10k5	C4	4n7 *	Q3	2N3904
R4	100R	C5	4n7 *	Q4	2N3904
R5	15k	C6	4U7	Q5	2N3904
R7	22k	C7	100n	Q6	2N3904
R9	15k	C8	4U7	Vactrol	VTL5C3
R10	47k5	C9	100p	IC1	LM358
R11	47k5	C11	100p	IC2	OP275
R12	47k5	C13	2u2	SW2	DPDT
R13	47k5	C14	100p	HiCut	DIP2
R15	1M	C15	4u7	VOL	100KA
R16	475R	C18	100n	COMP	100KB
R17	475k	C19	10n	EQ	50KB
R18	470k	C20	10n		
R19	4k7	C21	2u2		
R20	6k8	C22	100n		
R22	100R	C25	3n3		
R23	470k	C26	15n		
R24	22k	C29	3n3		
R25	100k	C30	100n		
R26	1k	C31	100n		
R27	3k3	D1	1N4001		
R28	470r	D3	1N4148		
R29	220k	D4	1N4148		
R30	470k	D5	1N4148		
R31	100k	D6	1N4148		
R32	220k	D7	1N4148		
R33	150k	D8	1N4148		
R34	470k				
R38	10k				


The bass version is run at 18v, presumably for more headroom. A madbeanpedals Road Rage or 3PRR would be ideal to use for this, running the 18v out of the RR to the 9v in on the ZiRCONiA pcb. Whether you use a Road Rage or a 3PRR, we recommend using LT1054 just to be safe, since the VTL5C3 draws 20mA on its own.

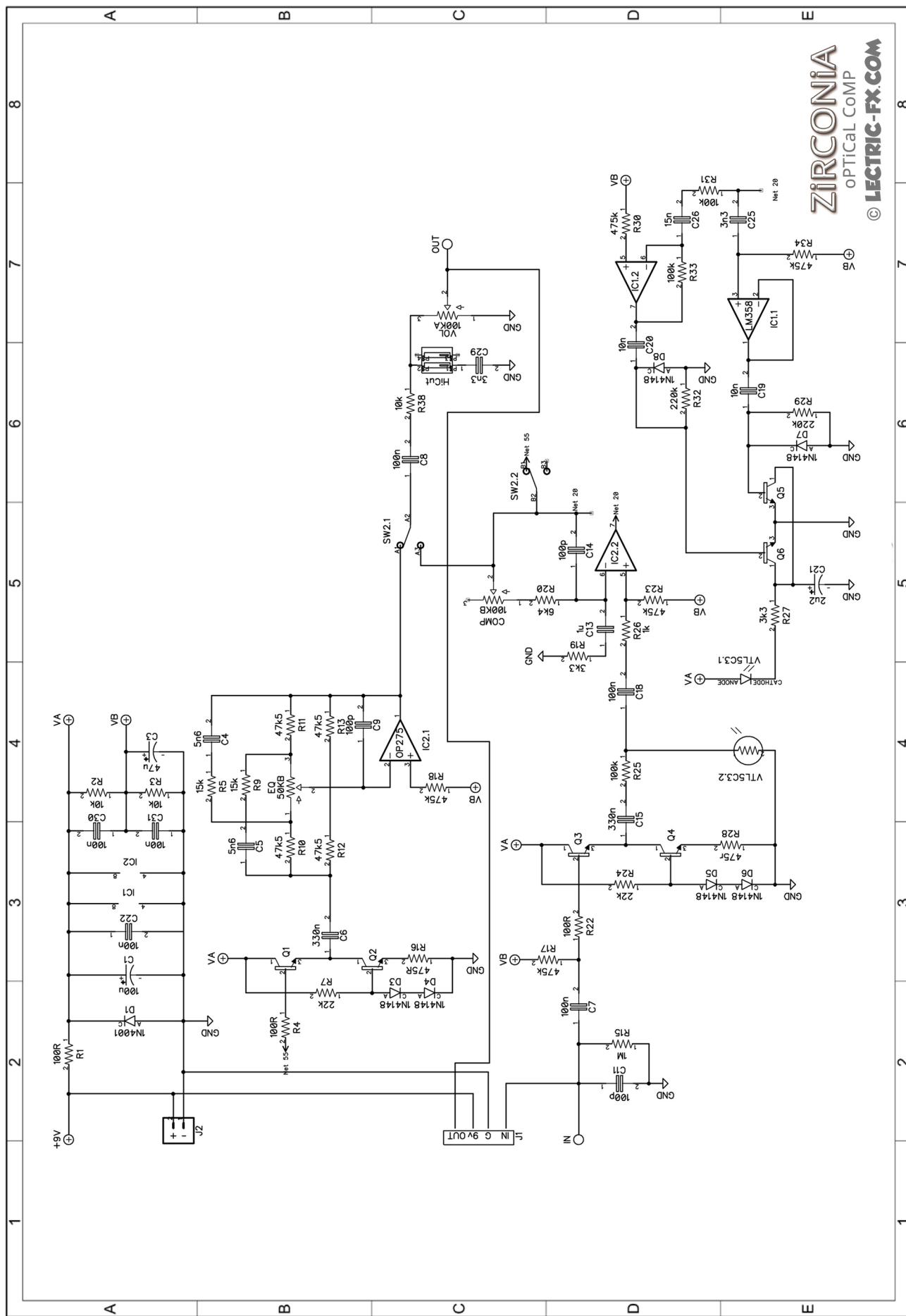\* These 2 caps decide the center frequency of the EQ control. They can be socketed for experimentation. The 4n7 values listed will give a center freq of 1060Hz, while a pair of 18n or 22n caps will be closer to 250Hz.



# Drill Guide Suggestion (Top Mount)

125b- Untested!

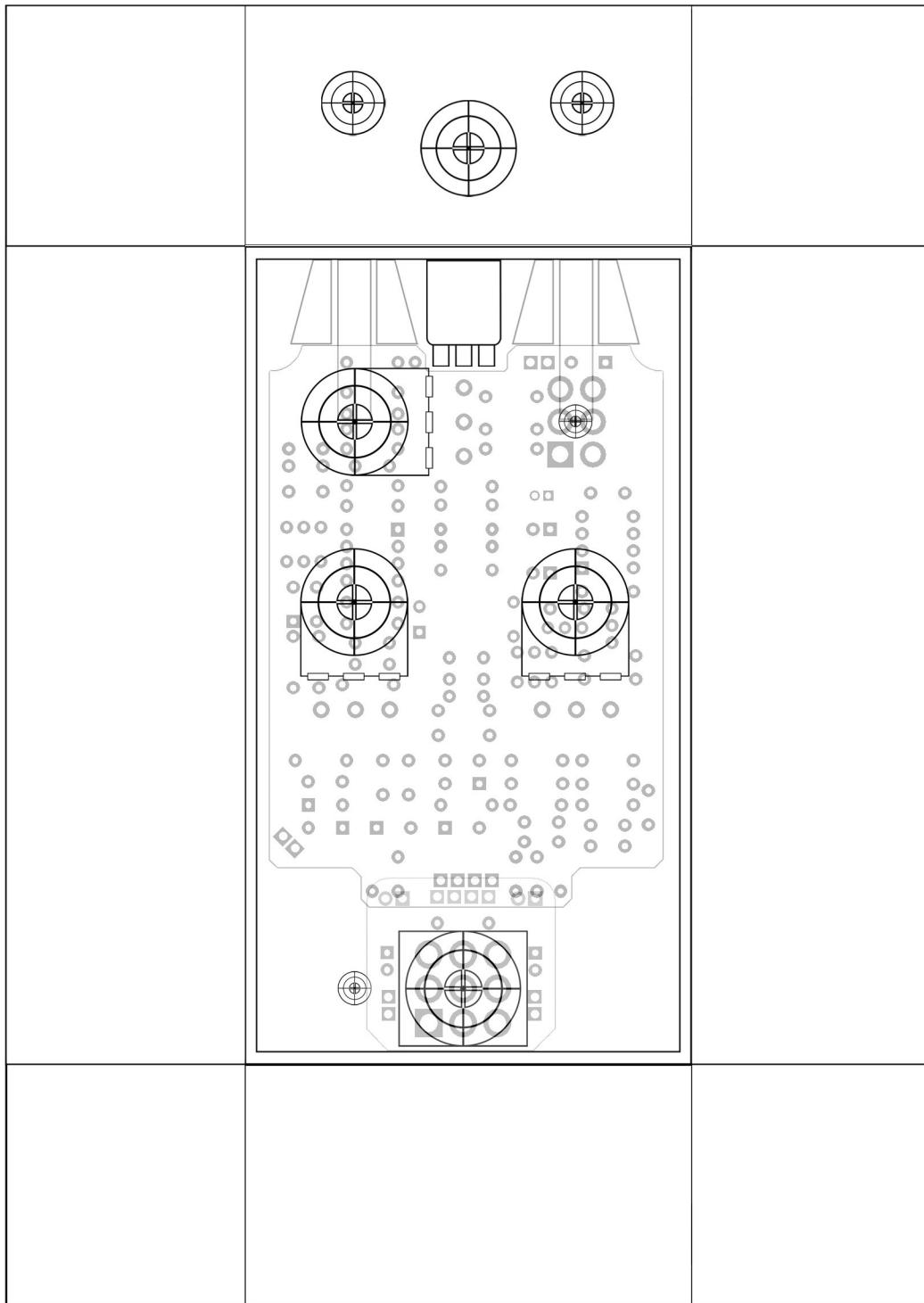

When using top mount jacks with the 3pdt pcb you may need to install D1, C13 and C15 on the backside.