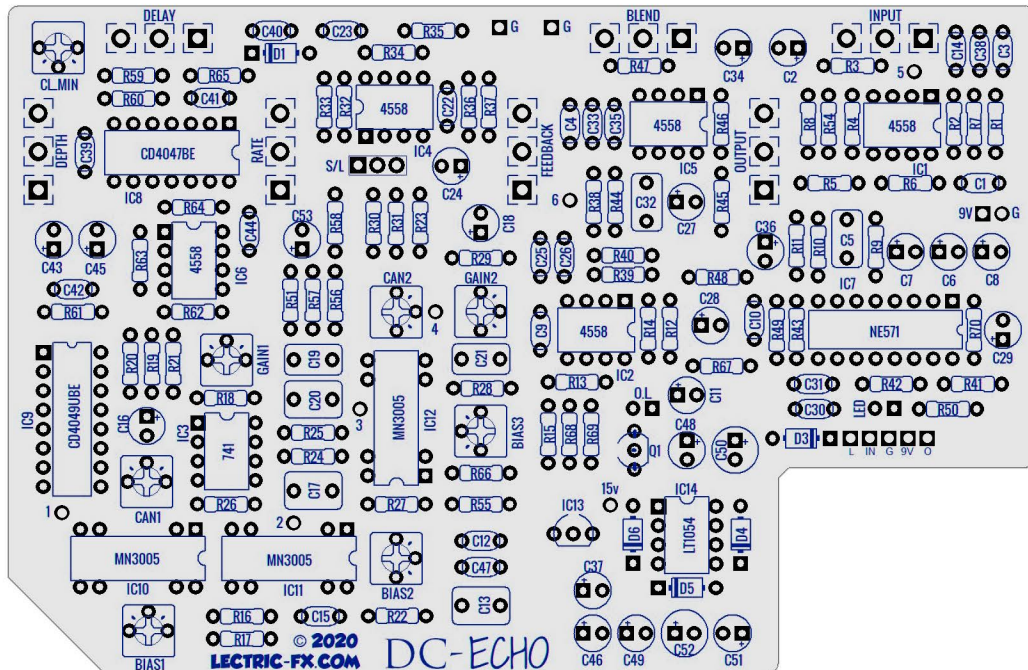


DC-ECHO

lectric-fx.com
07/21/2020



The Electro-Harmonix™ Echo 600 was released in approximately 1981 at the beginning of EHX's financial, union, & MN3005 supply woes, followed by their eventual bankruptcy. As such, it had a very short life cycle and few original units seem to circulate today. Its original price tag (\$339, nearly \$1000 with inflation vs the Deluxe Memory Man's™ \$219) may also be a reason behind this.

The circuit seems to have been designed from the standpoint of getting the absolute best performance from the MN3005 BBD chips in terms of functionality (offering control over every parameter compared to the Deluxe Memory Man's™ limited feature set), fidelity and noise. Released just before the 2 & 16 second digital delay, it may have been an attempt to offer a budget alternative when digital delay was just starting to take off in the consumer market, but still carried a hefty price tag.

Thankfully, we were given the chance to study an original unit, and this leads us to the Letric-FX DC-Echo, a faithful reproduction of this extremely rare unit.

So what does it sound like? In short, imagine a cleaner, brighter and quieter version of the Deluxe Memory Man™ that retains its legendary BBD chip warmth, then adds some handy extra features and additional delay time.

WARNING: This is an extremely complex build, do not attempt this as a first analogue delay effect and be confident of your soldering skills, biasing game and debugging abilities before attempting it. Even veteran builders should be sure to read this document thoroughly and double check all errata before continuing.

Attention: If you purchased a 1st run DC-ECHO PCB (identified by the lack of a version number) this will require the Input, Output & Delay pots to be wired in reverse for normal operation.

*Additionally, test points 5 & 6 on this circuit board version should be ignored, when following the biasing procedure, this now refers to IC7 (NE571) pin 7 (test point 5) & 15 (test point 6).

This has been corrected on all version numbered circuit boards and can be ignored. Apologies for any inconvenience.

Controls:

Input- Controls guitar/instrument level. Best set to just before the point of clipping with normal playing.

Output- Controls the circuit output level. This is used to match the effect level to bypass.

Blend- Blends the output signal between no effect (100% dry) to delay only (100% wet).

Feedback- Controls the number of repeats.

Rate- Controls the speed of the modulation from slow chorus to fast vibrato.

Depth- Controls depth of the modulation.

Delay- Adjusts the delay time of the effect from approximately 20mS (short mode) to 600mS (long mode).

Short/Long Switch- Selects between 1 (slap back delays up to 200mS) or all 3 MN3005 being active in circuit.

Biasing Procedure (No Scope):

Before you begin, you will need a signal source to input to the pedal (guitar, looper, cd player etc.) an audio probe and a frequency counter (scope or multimeter). You may find that using headphones instead of listening through a speaker cabinet will help with the procedure (although please be wary of levels in case of run away oscillation).

Control Settings:

Input - Insert your signal source to the effect and adjust this control until overload LED is dimly on. With a varying signal level such as a guitar there will be some flicker.

Output - 50%

Blend - CW

Feedback - CCW

Rate - CCW

Depth - CCW

Delay - CW

Short/Long - Short Position

You should begin by setting all trimmers to their halfway points.

Power on the unit and using your frequency counter, probe Test Point 1 and adjust the CL-Min trimmer until you read a frequency of 10kHz.

Set your multimeter aside.

Now, set Delay - CCW and with your input signal connected, audio probe Test Point 2 and adjust BIAS1 for the least amount of clipping/cleanest signal (You may need to reduce the input level if you cannot set this clean or increase it if you cannot hear the optimal bias point).

After adjusting BIAS1, move on to adjusting GAIN1 to achieve an equal signal level at Test Points 5 & 6. *

You should now switch the toggle to the Long setting and audio probe Test Point 3.

Adjust BIAS 2 for the least amount of clipping/cleanest signal and then move on to Test Point 4 and adjust BIAS3. Again, for the least amount of clipping/cleanest signal.

Once you have finished with BIAS 2 & 3, move on to GAIN 2 and once again adjust for equal signal level at Test Points 5 & 6*.

After completion of the BIAS & GAIN trimmer settings, you should now set the Delay Control CW and disconnect your input signal source.

Audio probe Test Point 2, you should hear a steady 10kHz tone. Adjust the CAN1 Trim until this tone is at its quietest point (there should be a small range of the trimmer where it is quieter and within this range you will have to very gently adjust for the optimal setting, preferably where it completely disappears although if complete silence is achievable will vary with set up).

Move your Audio Probe on to Test Point 4 and adjust the CAN2 Trim, repeating the same procedure as with CAN1.

Finally, it's time to test the pedal is functioning correctly. Set Delay CCW, plug in your guitar (or other instrument) and adjust the input level to the point before normal playing produces clipping and the output level to match your bypass signal. Check that you have equal signal level at both extremes (CW & CCW) of the blend pot in both short and long delay modes and that all other controls are working as expected.

You have now completed the biasing procedure.

* See 'Attention' Section.


Be advised: For this one project we will not be providing a schematic, and ask that you please understand and respect this, as we have to respect our collaborator's wishes to continue bringing out the projects that no one else offers.

If you get stuck, please post over at the LECTRIC-FX subforum on madbeanpedals.com/forum and one of our team will get to you.


For troubleshooting purposes, this is your Wet Signal Audio Probing Flow (in Long Mode): IC1 Pin 1 - IC1 Pin 7 - IC7 Pin 7 - IC2 Pin 7 - TP2 (IC10) - IC3 Pin 6 - TP3 (IC11) - TP4 (IC12) - IC2 Pin 1 - IC4 Pin 7 - IC4 Pin 1 - IC7 Pin 10 - IC5 Pin 7

I had to go through this procedure a handful of times before I achieved satisfactory results, so be warned it's a tricky go. Remember that you are setting the bias and levels of 3 series MN3005 here so poor biasing, especially at the start of the procedure, will accumulate and magnify problems at the end in 'long' mode. Listen carefully, take your time and don't be afraid to step away.

Part Numbers

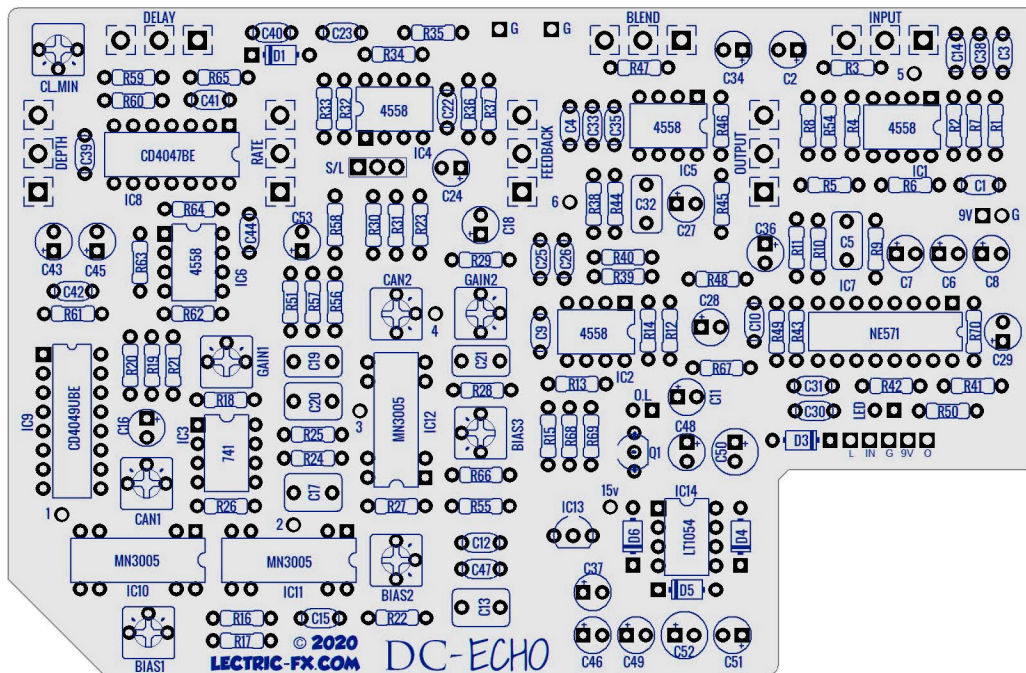

Values

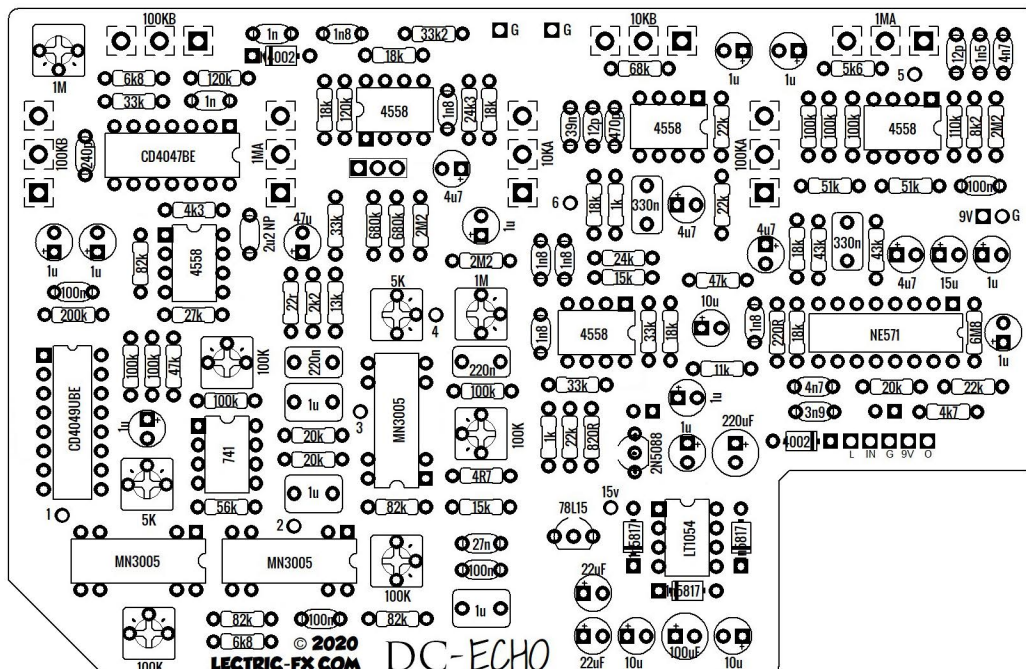

lectric-fx.com
Complete BOM:

Resistors	Values	Resistors	Values	Caps	Values	Diodes	Values
R1	2M2	R56	13k	C1	100n	D1	1n4001
R2	110k	R57	2k2	C2	1u	D3	1n4002
R3	5k6	R58	33k	C3	4n7	D4	1n5817
R4	100k	R59	6k8	C4	39n	D5	1n5817
R5	51k	R60	33k	C5	330n	D6	1n5817
R6	51k	R61	200k	C6	15u		
R7	8k2	R62	27k	C7	4u7	O.L. LED	*
R8	100k	R63	82k	C8	1u	LED	Preference
R9	43k	R64	4k3	C9	1n8		
R10	43k	R65	120k	C10	1n8	ICs	Values
R11	18k	R66	4R7	C11	1u	IC1	NJM4558
R12	18k	R67	11k	C12	27n	IC2	NJM4558
R13	33k	R68	22k	C13	1u NP	IC3	LM741
R14	33k	R69	820R	C14	12p	IC4	NJM4558
R15	1k	R70	6M8	C15	100n	IC5	NJM4558
R16	82k			C16	1u	IC6	NJM4558
R17	6k8			C17	1u NP	IC7	NE571
R18	100k			C18	1u	IC8	CD4047BE
R19	100k			C19	220n	IC9	CD4049UBE
R20	100k			C20	1u NP	IC10	MN3005
R21	47k			C21	220n	IC11	MN3005
R22	82k			C22	1n8	IC12	MN3005
R23	2M2			C23	1n8	IC13	LM78L15
R24	20k			C24	4u7	IC14	LT1054
R25	20k			C25	1n8		
R26	56k			C26	1n8	Transistors	Values
R27	82k			C27	4u7	Q1	2N5088
R28	100k			C28	10u		
R29	2M2			C29	1u	Switches	Values
R30	680k			C30	3n9	SW1 Toggle	SPDT
R31	680k			C31	4n7		
R32	120k			C32	330n	Trimmers	3362 Type
R33	18k			C33	120n	GAIN1	100K
R34	18k			C34	1u	GAIN2	1M
R35	33k2			C35	470p	BIAS1	100K
R36	24k3			C36	4u7	BIAS2	100K
R37	18k			C37	22uF	BIAS3	100K
R38	18k			C38	1n5	CAN1	5K
R39	15k			C39	240p	CAN2	5K
R40	24k			C40	1n	CL_MIN	1M
R41	22k			C41	1n		
R42	20k			C42	100n	Pots	PC Mount
R43	18k			C43	1u	BLEND	10KB
R44	1k			C44	2u2 NP	DELAY	100KB
R45	22k			C45	1u	DEPTH	100KB
R46	22k			C46	22uF	FEEDBACK	10KA
R47	68k			C47	100n	RATE	1MA
R48	47k			C48	1u	INPUT	1MA
R49	220R			C49	10u	OUTPUT	250KA
R50	4k7			C50	220uF		
R51	22r			C51	10u		
R54	100k			C52	100uF		
R55	15k			C53	47u		

← CLR for LED

* This LED should preferably have fV between 1.8 - 2.1V

Quantity	Value	Quantity	Value	Quantity	Value
1	4R7	2	51k	1	12p
1	22R	1	56k	1	240p
1	220R	1	68k	1	470p
1	820R	4	82k	2	1n
2	1k	7	100k	1	1n5
1	2k2	1	110k	6	1n8
1	4k3	2	120k	1	3n9
1	4k7	1	200k	2	4n7
1	5k6	2	680k	1	27n
2	6k8	3	2M2	1	39n
1	8k2	1	6M8	4	100n
1	11k			1	120n
1	13k			2	220n
2	15k			2	330n
7	18k			3	1u NP
3	20k			10	1u
4	22k			1	2u2 NP
1	24k			4	4u7
1	24k3			3	10u
1	27k			1	15u
4	33k			2	22u
1	33k2			1	47u
2	43k			1	100u
2	47k			1	220u

Voltages:

PSU reading=9.25V, 15V test point=15.13V. All knobs at noon.

IC1

Pin #	V
1	7.58
2	7.6
3	7.58
4	0
5	7.58
6	7.58
7	7.58
8	15.13

IC2

Pin #	V
1	7.58
2	7.58
3	7.56
4	0
5	6.89
6	6.91
7	6.91
8	15.13

IC3

Pin #	V
1	0
2	5.6
3	5.6
4	0
5	0
6	5.6
7	15.13
8	.01

IC4

Pin #	V
1	7.58
2	7.59
3	7.58
4	0
5	7.58
6	7.58
7	7.58
8	15.13

IC5

Pin #	V
1	7.63
2	7.59
3	7.58
4	0
5	7.51
6	7.53
7	7.53
8	15.13

IC7

Pin #	V
1	1.06
2	1.81
3	1.81
4	0
5	1.81
6	1.81
7	6.91
8	1.81
9	1.81
10	7.53
11	4.7
12	1.81
13	15.13
14	1.81
15	1.81
16	0.6

IC8

Pin #	V
1	8.0
2	7.1
3	7.1
4	15.12
5	15.11
6	15.11
7	0
8	0
9	0
10	7.55
11	7.55
12	0
13	8.0
14	15.12

IC9

Pin #	V
1	15.12
2	7.52
3	7.55
4	7.52
5	7.55
6	7.52
7	7.55
8	0
9	7.55
10	7.52
11	7.55
12	7.52
13	0
14	7.55
15	7.51
16	0

IC6

Pin #	V
1	flux
2	7.58
3	flux
4	0
5	7.58
6	7.59
7	flux
8	15.11

IC10

Pin #	V
1	15.13
2	7.52
3	5.5
4	5.5
5	0
6	7.57
7	7.82
8	1

IC11

Pin #	V
1	15.12
2	7.52
3	6.77
4	6.77
5	0
6	7.51
7	7.96
8	1

IC12


Pin #	V
1	15.12
2	7.52
3	4.6
4	4.6
5	0
6	7.51
7	6.8
8	1

Q1: C = 13.6V, B = 0, E = 0


WIRING SUGGESTION

A miniature 3pdt footswitch pcb will be provided with each DC-Echo pcb sold, at no extra cost (provided it's in stock). You can use it to aid in wiring if you choose, or just use your favorite true-bypass wiring scheme instead.

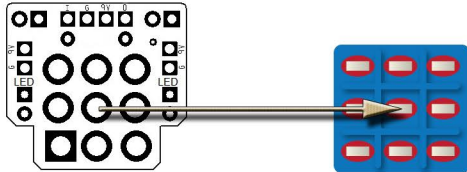The CLR (current-limiting resistor) and bypass LED are both on the pcb in this case, so all you have to do is wire the mini pcb to the larger pcb. Make sure the square pad is in the bottom left corner as shown (and the silkscreen of the resistor is facing away so you don't see it).



INNER VIEW OF BOX

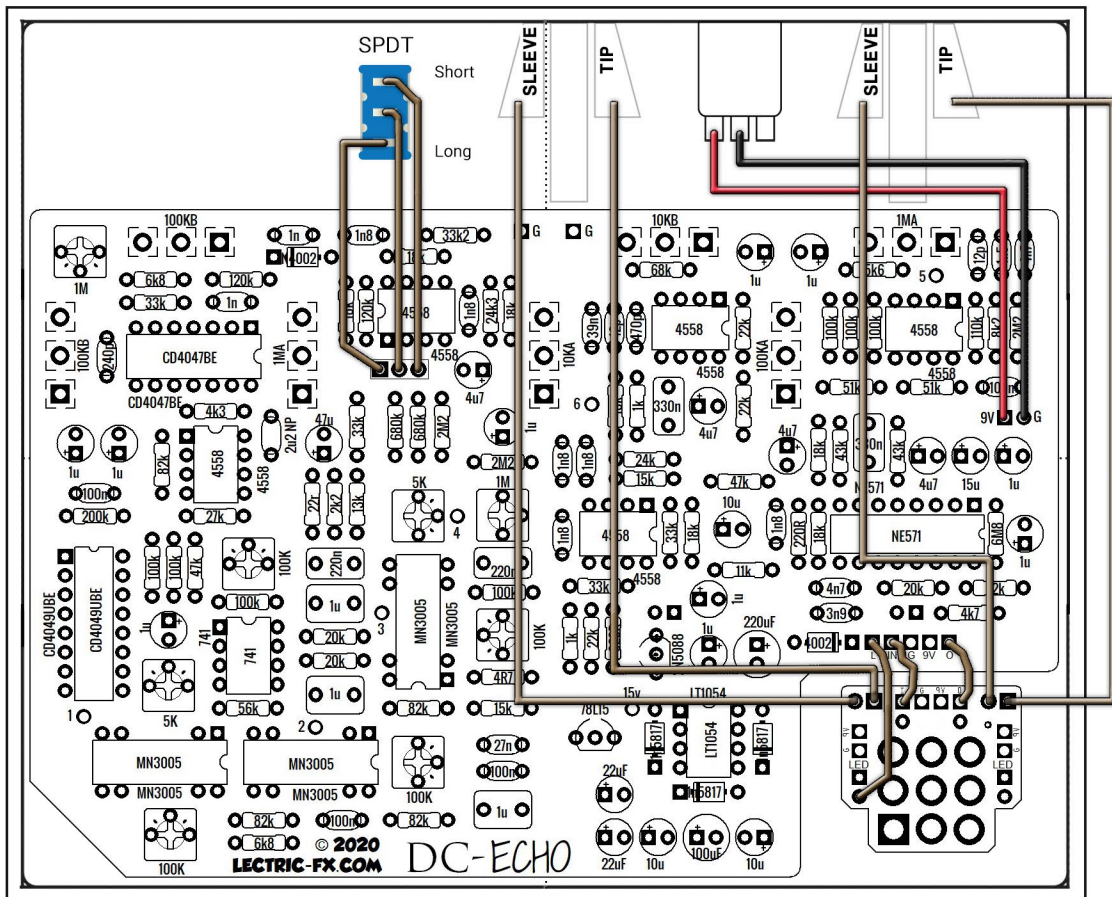

You can twist each of the 2 pairs of wires coming off the mini 3pdt pcb together with a drill if you want, and run them under the pcb up to the tips and sleeves of the in/out jacks, for a very clean look.

